

Reverse Classroom: Op Amps Quiz 2

REV 0; August 18, 2019

1 Golden Rules vs. the Diff-Amp View of an Op Amp

Now you know that an op amp is “simply” a very good difference amp: one with

- lots of gain;
- high R_{in} ;
- low R_{out}

If we extrapolate these parameters to their most favorable limit, we get the:


Perfect Op Amp Design Rules

1. No current flows into or out of the inputs (V_- and V_+) of an op amp.
2. If there is negative feedback, the op amp keeps the negative input at the same voltage as the positive input, so you can assume that $V_- = V_+$.
3. The inputs of an op amp should always be kept between V_{CC} and V_{EE} (i.e., $V_{EE} \leq V_-, V_+ \leq V_{CC}$).
4. The output of an op amp cannot be greater than V_{CC} or less than V_{EE} .

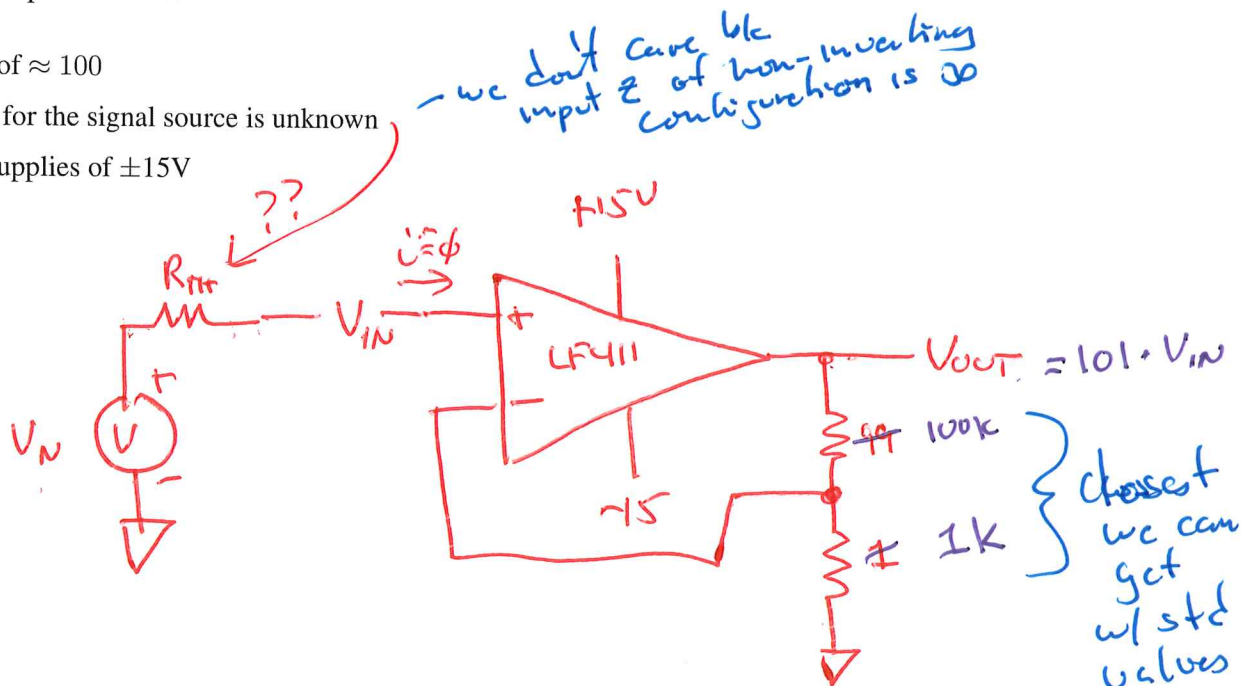1.1 Design

Apply the Golden Rules to design a non-inverting amp using an LF411 op amp. Use standard value resistors. Here are the specifications:

- gain of ≈ 100
- R_{out} for the signal source is unknown
- use supplies of $\pm 15V$



1.2 Amplifier Input Impedance

What is the input impedance of your amplifier according to the golden rules?

$$\hat{v}_{in} = \phi \quad \frac{v_{in}}{i_{in}} = \infty$$

1.3 Amplifier Output Impedance

What is the approximate output impedance of your amplifier?

$$\approx \phi \Omega$$

1.4 ...analyzed according to the golden rules...

According to the golden rules, what is the voltage difference between the two op amp terminals, marked “+” and “-”? (Assume an input signal of 0.1V)

$$V_+ = V_- \\ (V_+ - V_-) = \phi V$$

1.5 ...analyzed according to your understanding of differential amplifiers...

Let's assume that the op amp's open-loop gain, A , is 10,000 (as it is, at some particular frequency).

According to your understanding of differential amplifiers, what is the voltage difference between the two terminals, marked “+” and “-”, if your design of §1.1 is fed an input signal of 0.1V?

$$\begin{aligned} V_o &= 10,000 (V_+ - V_-) \\ V_- &= V_o \cdot \frac{1k}{1k + 100k} \approx \frac{V_o}{101} \quad V_o \approx 101 \cdot V_- \\ 101 \cdot V_- &= 10,000 (V_+ - V_-) = 10,000 V_+ - 10,000 V_- \\ V_- (10,000 + 101) &= 10,000 V_+ \\ 10101 \cdot V_- &= 10,000 V_+ \\ V_- &= \frac{10,000}{10,101} V_+ \quad \text{so if } V_+ = 0.1V \\ V_- &= 0.099V \end{aligned}$$


Now complete Lab 6 through part 6L.4

$$V_+ - V_- \approx 1mV$$

The Inverting Configuration

$$\frac{0V - V_{out}}{100k} = \frac{-V_{out}}{100k}$$

PART III
PAGE 1

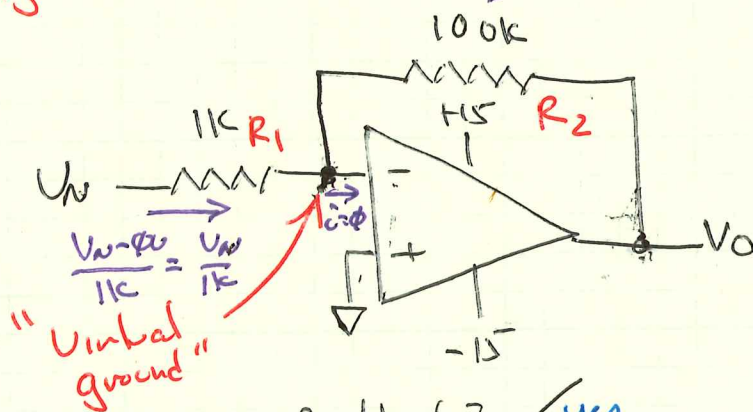

$$\frac{V_{in}}{1k} = \frac{-V_{out}}{100k}$$

$$\frac{V_{out}}{V_{in}} = -\frac{100k}{1k} = -100$$

neg feedback? ☒ yes

$$V_+ = V_- \text{ but } V_+ = 0V \text{ so } V_- = 0V$$


inverting gain of 100 amplifier
(inverting configuration)

$$G = -\frac{R_2}{R_1}$$

What is the input impedance of the inverting configuration?

$$\frac{V_{in}}{I_{in}} = \frac{V_{in}}{\frac{V_{in}}{R_1}} = R_1$$

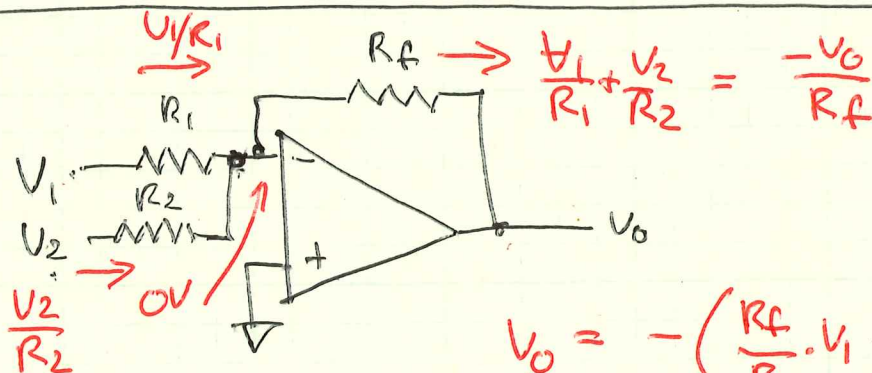even though op amp has very high input Z , the circuit does not




$$\frac{V_1}{R_1} + \frac{V_2}{R_2} = \frac{-V_o}{R_f}$$

$$V_o = -\left(\frac{R_f}{R_1} \cdot V_1 + \frac{R_f}{R_2} \cdot V_2\right)$$

we can add as many inputs as we want to sum multiple voltages


Inverting

Summing amplifier

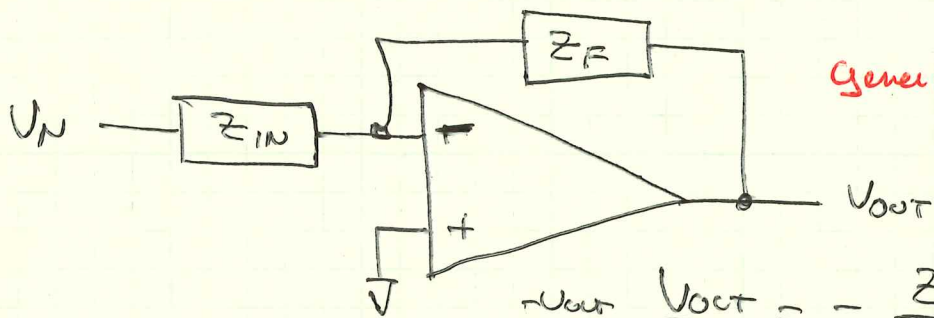

Generic inverting configuration
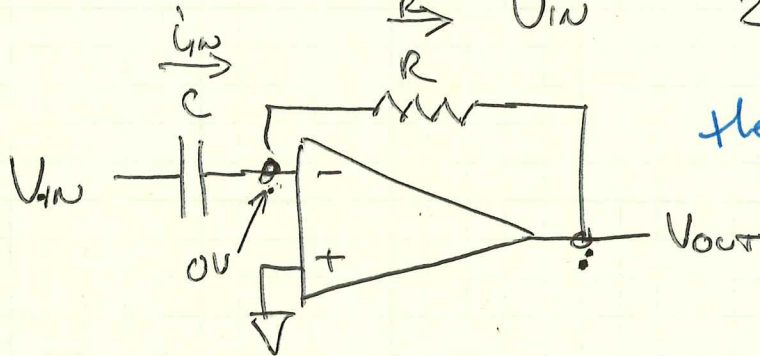
$$\frac{V_{OUT}}{V_{IN}} = - \frac{Z_F}{Z_{IN}}$$



there is neg feedback ✓


Op amp differentiator

$$i = C \frac{dV}{dt}$$

$$i_{IN} = C \frac{dV_{IN}}{dt} = - \frac{V_{OUT}}{R}$$


$$V_{OUT} = -RC \frac{dV_{IN}}{dt}$$

Inverting differentiator

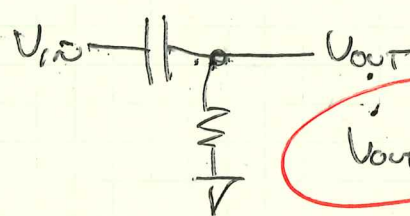

fixes this

$$V_{OUT} \ll V_{IN}$$

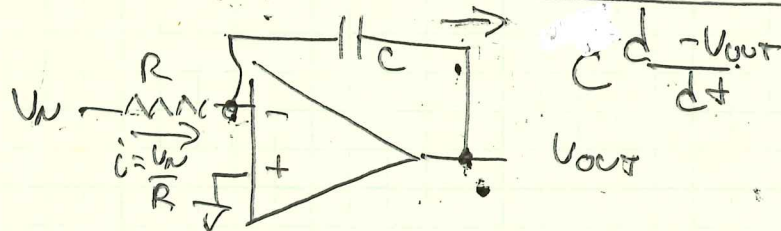

there is neg feedback (except at DC)

$$\frac{V_{IN}}{R} = -C \frac{dV_{OUT}}{dt}$$

Inverting integrator

$$V_{IN} = -RC \frac{dV_{OUT}}{dt}$$

$$V_{OUT} = -\frac{1}{RC} \int V_{IN} dt$$

fixes this

$$V_{OUT} \ll V_{IN}$$