

# Reverse Classroom: Op Amps Quiz 2

REV 0; August 18, 2019

## 1 Golden Rules vs. the Diff-Amp View of an Op Amp

Now you know that an op amp is “simply” a very good difference amp: one with

- lots of gain;
- high  $R_{in}$ ;
- low  $R_{out}$

If we extrapolate these parameters to their most favorable limit, we get the:

### Perfect Op Amp Design Rules

1. No current flows into or out of the inputs ( $V_-$  and  $V_+$ ) of an op amp.
2. If there is negative feedback, the op amp keeps the negative input at the same voltage as the positive input, so you can assume that  $V_- = V_+$ .
3. The inputs of an op amp should always be kept between  $V_{CC}$  and  $V_{EE}$  (i.e.,  $V_{EE} \leq V_-$ ,  $V_+ \leq V_{CC}$ ).
4. The output of an op amp cannot be greater than  $V_{CC}$  or less than  $V_{EE}$ .

### 1.1 Design

Apply the Golden Rules to design a non-inverting amp using an LF411 op amp. Use standard value resistors. Here are the specifications:

- gain of  $\approx 100$
- $R_{out}$  for the signal source is unknown
- use supplies of  $\pm 15V$

## 1.2 Amplifier Input Impedance

What is the input impedance of your amplifier according to the golden rules?

## 1.3 Amplifier Output Impedance

What is the approximate output impedance of your amplifier?

## 1.4 ...analyzed according to the golden rules...

*According to the golden rules*, what is the voltage difference between the two op amp terminals, marked “+” and “-”? (Assume an input signal of 0.1V)

## 1.5 ...analyzed according to your understanding of differential amplifiers...

Let's assume that the op amp's open-loop gain,  $A$ , is 10,000 (as it is, at some particular frequency).

According to your understanding of differential amplifiers, what is the voltage difference between the two terminals, marked “+” and “-”, if your design of §1.1 is fed an input signal of 0.1V?

Now complete Lab 6 through part 6L.4